

### **Objective:**

Design, fabrication, implementation of a 150 W, 100 V to 230 V and 100 V to 50V, 20 kHz Buck-Boost converter.

$$V_{in} = 100V$$

$$V_o = (V_{in} \times D) / (1-D)$$

Step up from 100 V to 230 V →  $D=23/33=69.7\%$

Step down from 100V to 50V →  $D=1/3=33.33\%$


### **Component Design**

Component	Value	Voltage rating	Current rating
Inductor	4 mH		5A
Capacitor	20uF	250V	
Switch	MOSFET IRF740	400V	10A
Diode	MUR860	Vr=600V, Vf=1.5V	If=8A, Ir=10uA

### **Simulation and component selection:**


- Simulation-based verification of the component ratings is **done** to ensure feasibility before fabrication.
- identified key components, including **MOSFETs, Diodes, Inductors, and Capacitors**, based on **desired voltage and current ratings**.
- Circuit layout using MATLAB feasibility before fabrication

# MATLAB SIMULATION

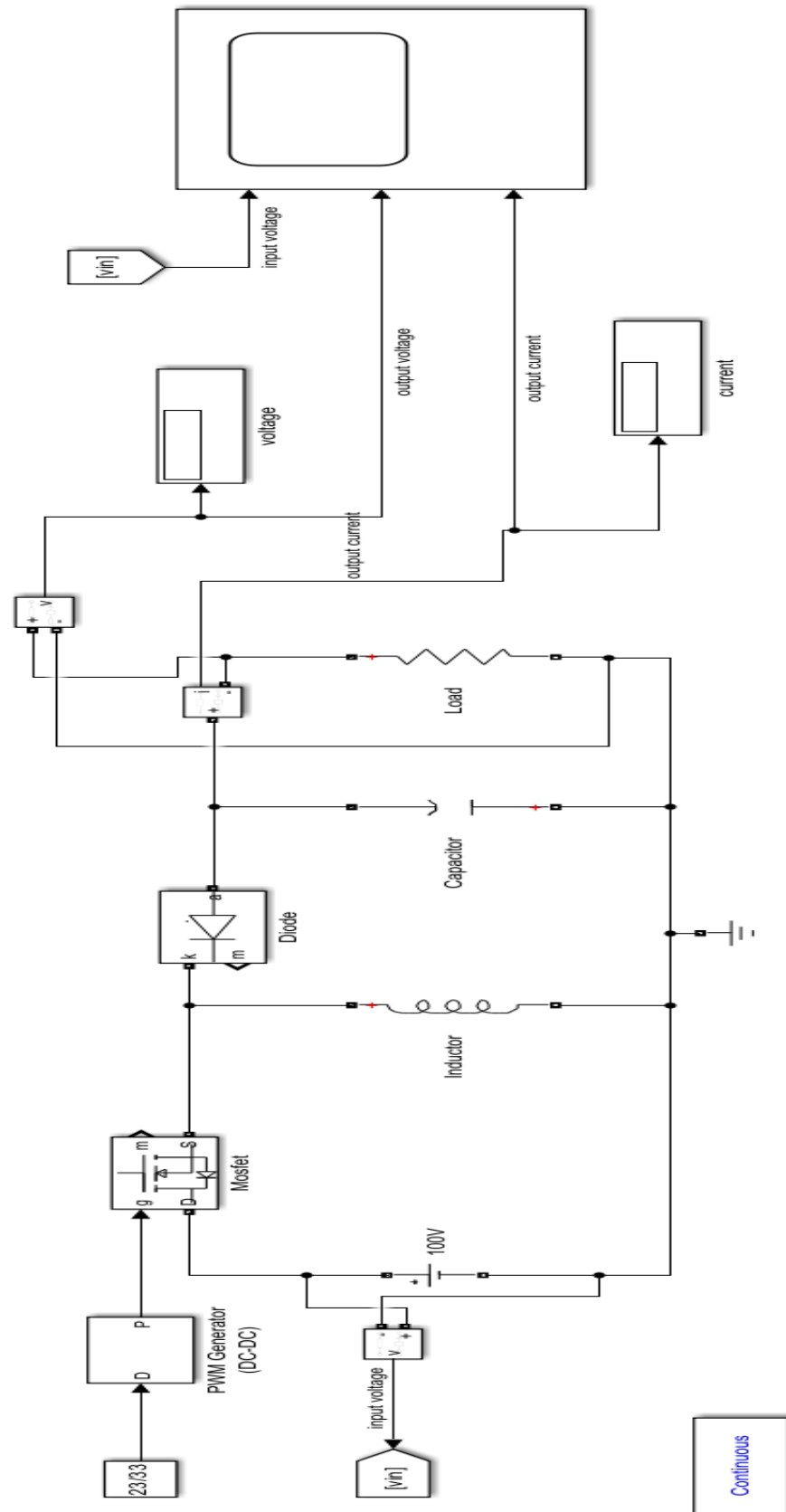


## Analytical waveforms

### Boost operation--


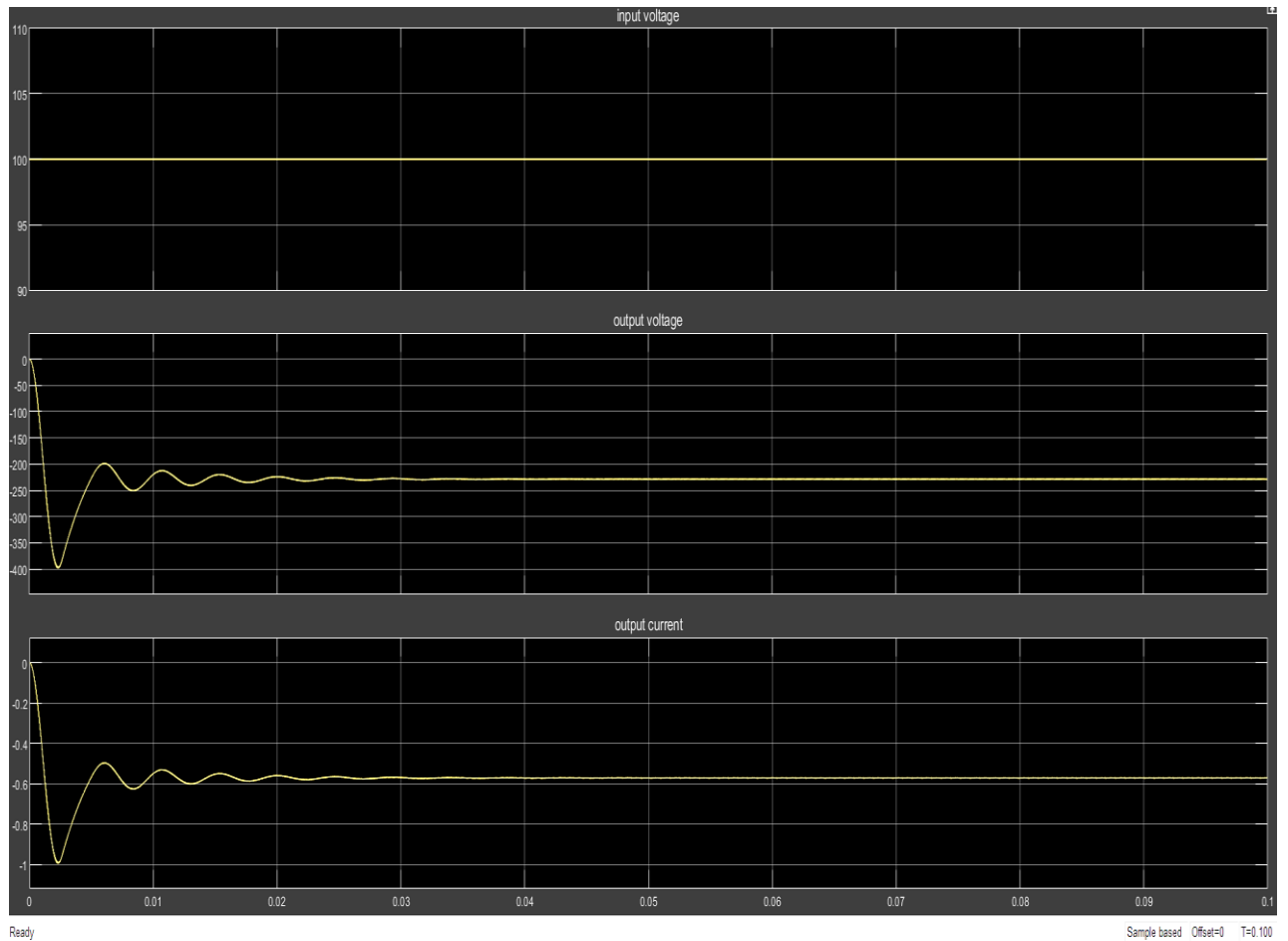



### Buck operation—

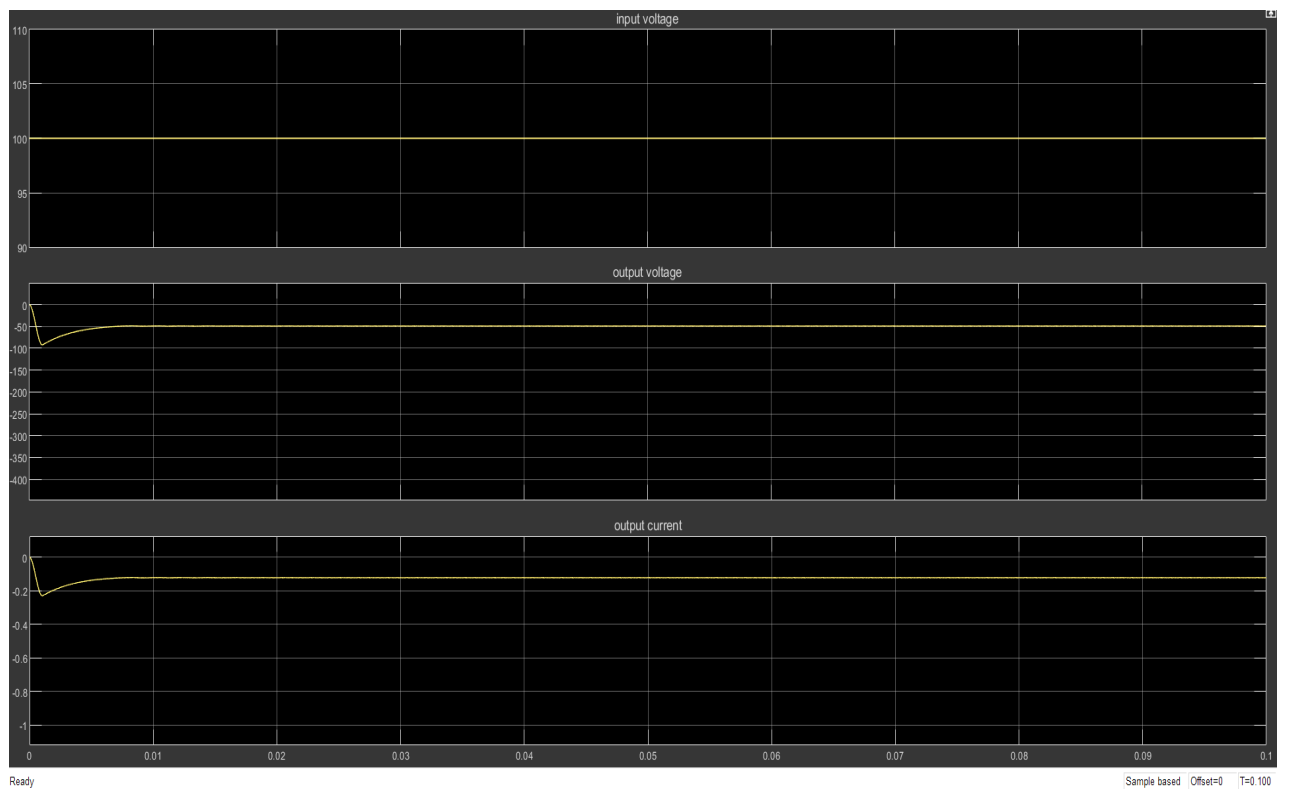

## PCB layout and design

Designed PCB Layout using Proteus

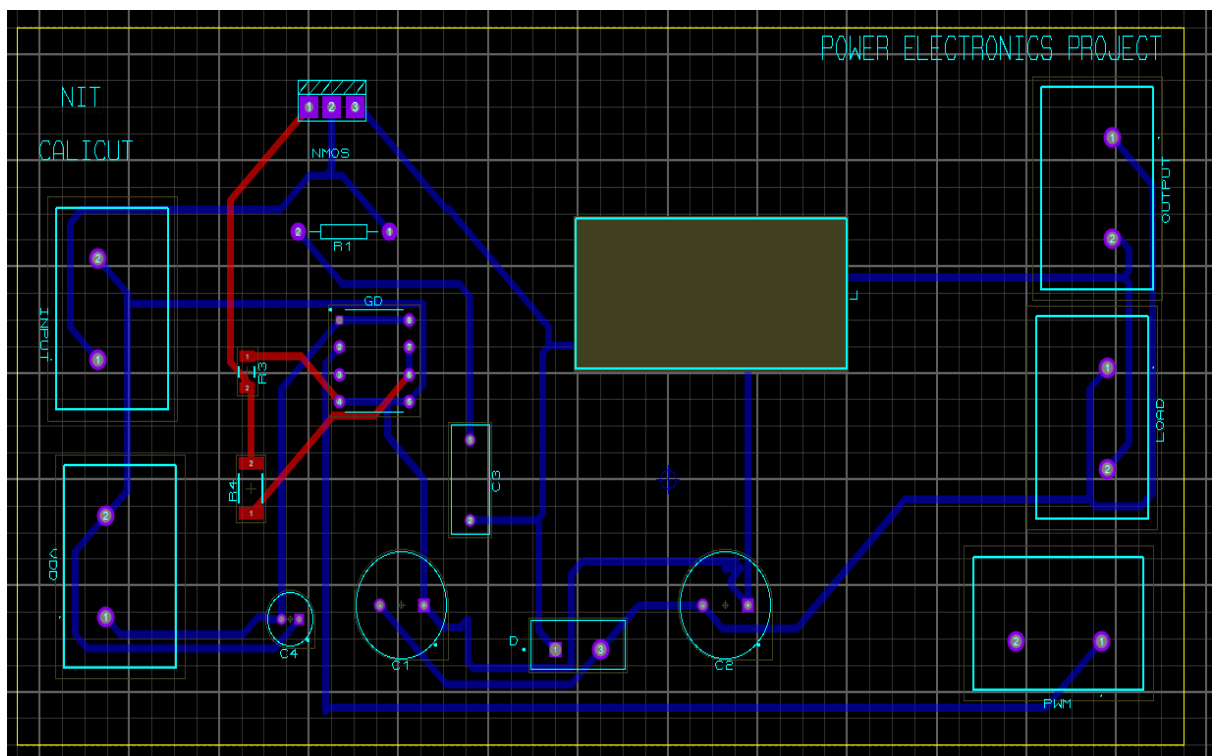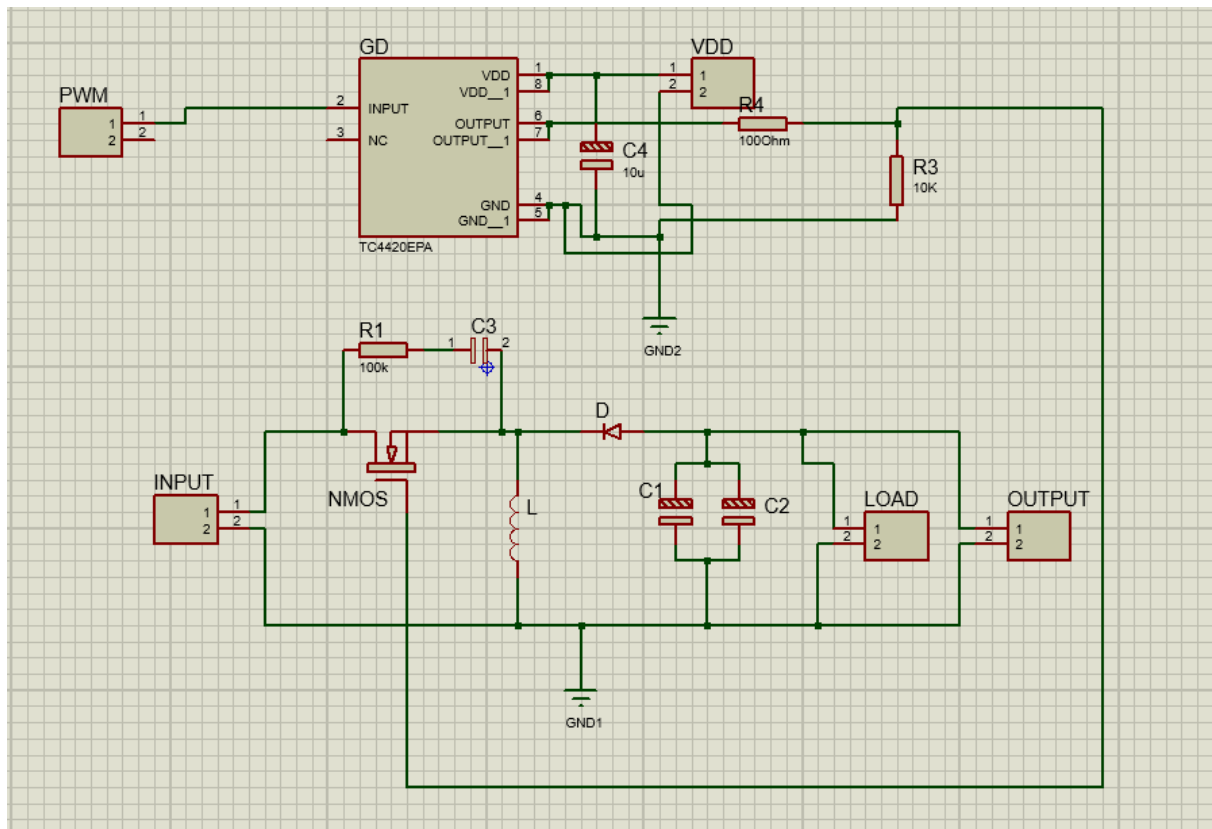

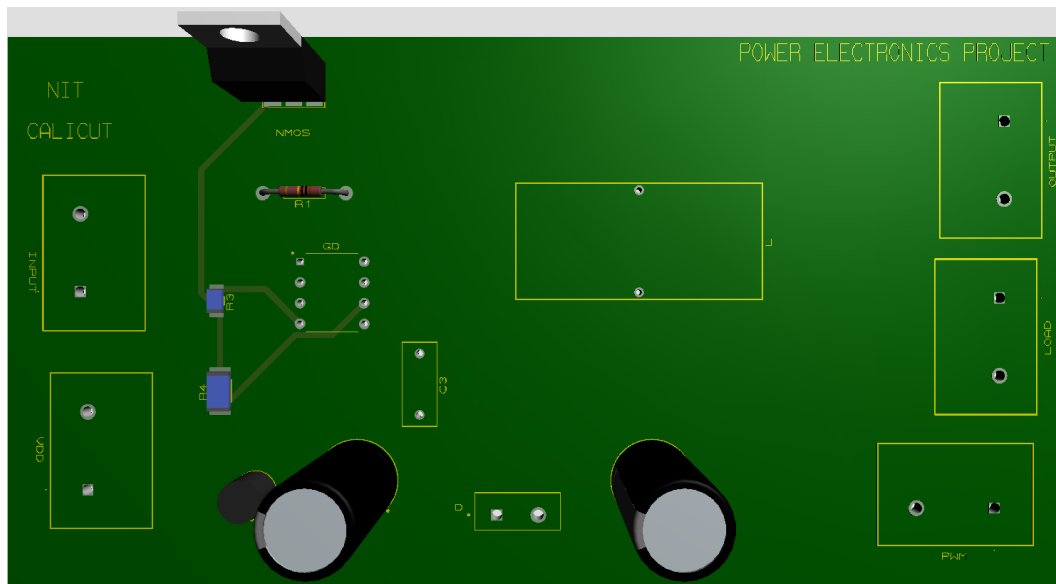

## PCB Specifications

### PCB Bare Board Specifications


		- Updated Specifications	
Dispatch Unit	Single Board	Panel By	-
Board Size	130.00 x 67.50 mm	Panel Qty	-
Repeat X	-	Repeat Y	-
PCB Per Panel	0	Different Design Per Panel	-
Distance b/w PCBs	-	Board Separation	-
Panel Dim	-	Panel Border	-
Material	FR4	Layers	2 L
Board Thickness	0.063 inch/1.6 mm	TG	Std. Tg (130-140 °)
Surface Finish	HASL (SnPb)	Finish Cu Thickness	70 µ/2 oz
Solder Mask Bottom	Green	Inner Cu Thickness	0 µ/0 oz
Solder Mask Top	Green	Legend Top	White
Legend Bottom	White	Blind & Buried via	No
Peel Off	No	Countersunk	No
Carbon Contacts	No	Hard Gold(Gold Tabs)	0.00
Manufacturing Logo	No	Serialization For PCB	No
Impedance Control	No	Viafill	No
ET Symbol	No	Special BuildUp	No
Round Edge Plating	No	Bevelling	No
UL Sign	No	Quality Standard	IPC-600A-CLASS-II
Data Approval	No	Microsection Report	No
Electrical Testing	Yes	Gold Area Top	0 %
Date Code	No	Gold Area Bottom	0 %
		Depth routing	No


### Buildup Image

Core-1.50 (0.035/0.035)

Total thickness - 1.640

## Pcb assembly :

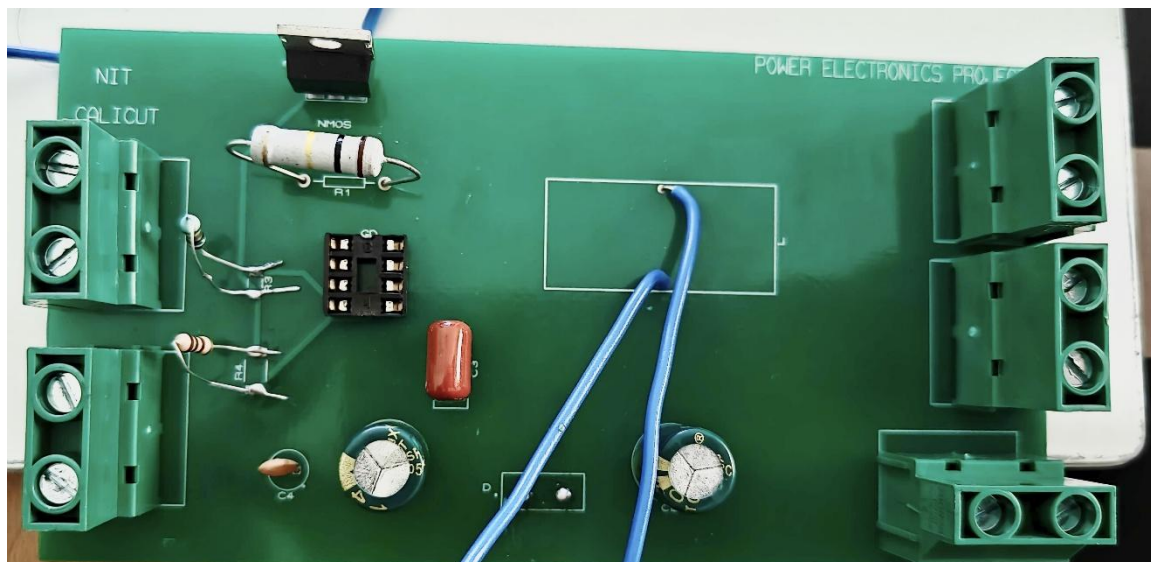

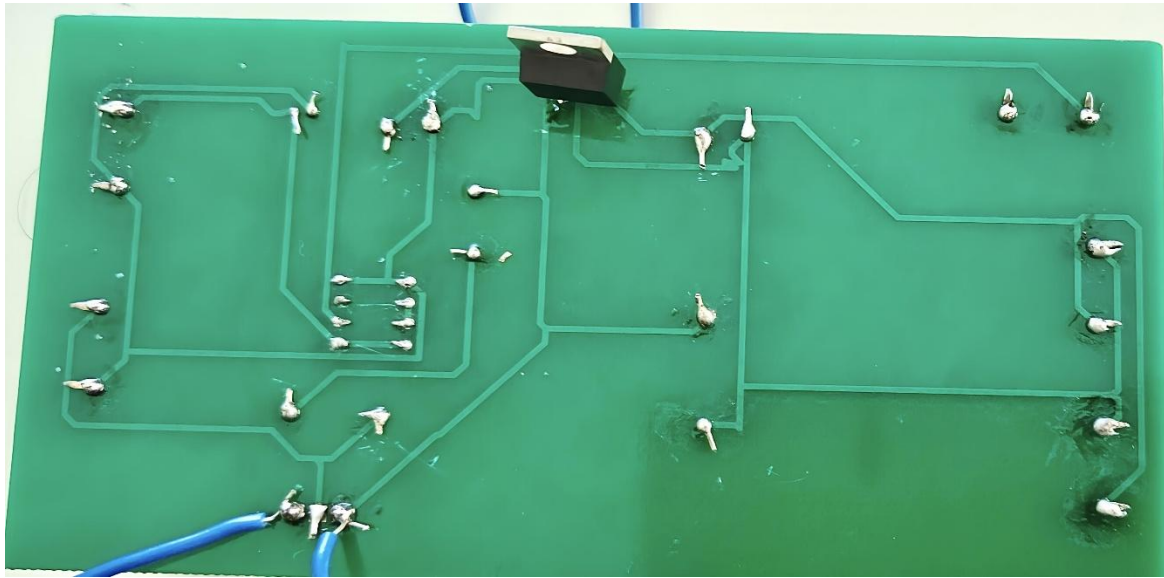

### Calculations:

- Boost:  $D = 230 / (230 + 100) = 0.697$
- Buck:  $D = 50 / (50 + 100) = 0.333$
- $\Delta i_L = 30\%$  of max current
- $\Delta V_o = 1\%$  of the output voltage

### Critical inductance:

$$L_{crit} = \frac{(1 - D)^2 \cdot R}{2f_s}$$

a) For Boost ( $D = 0.697$ )

$$L_{crit} = \frac{(1 - 0.697)^2 \cdot 350}{2 \cdot 20000} = \frac{(0.303)^2 \cdot 350}{40000} \approx \frac{32.17}{40000} = 0.804 \text{ mH}$$

b) For Buck ( $D = 0.333$ )

$$L_{crit} = \frac{(1 - 0.333)^2 \cdot 350}{2 \cdot 20000} = \frac{(0.667)^2 \cdot 350}{40000} \approx \frac{155.7}{40000} = 3.89 \text{ mH}$$

**Conclusion:**

Using  $4 \text{ mH} > L_{crit}$  in both modes, so the converter operates in Continuous Conduction Mode (CCM)

### Capacitance calculation :

Capacitance is calculated from below formula

$$C = (I_o \times D) / (\Delta V_o \times f_s)$$

$$\text{Critical capacitance } C_c = D / (2 \times f \times R_L)$$

After the calculation, it is found to be  $10 \mu\text{F}$ , but through simulation it is

chosen to be 20uF for better accuracy

### **Component Ordering:**

<b>NMOS</b>	-IRF740
<b>Diode</b>	-MUR860
<b>Gate Driver</b>	-TLP250
<b>RC snubber</b>	-100k $\Omega$ (carbon film) + 0.1uF (ceramic capacitor)
<b>Inductor</b>	- 4mH
<b>Capacitor</b>	- 20uf, 400v(electrolytic capacitors)
<b>Load resistor</b>	- 350 $\Omega$

### **Micro Controller for gate pulse:**

#### **Arduino Uno R3:**


- Used Timer1 in Phase Correct PWM mode.
- PWM frequency ~20 kHz.
- Oscilloscope used to verify PWM pulse width and frequency.
- Generated pulses at output pins 9 and 10

#### **Code for pulse generation:**


```
void setup() {  
  // Set D9 and D10 as output  
  pinMode(9, OUTPUT);  
  pinMode(10, OUTPUT);  
  
  // Stop Timer1  
  TCCR1A = 0;  
  TCCR1B = 0;  
  TCNT1 = 0;  
  
  // Set Fast PWM mode with ICR1 as TOP  
  // WGM13:WGM10 = 14 => Fast PWM with ICR1 as TOP  
  TCCR1A |= (1 << COM1A1) | (1 << COM1B1); // Non-inverting mode  
  TCCR1A |= (1 << WGM11);  
  TCCR1B |= (1 << WGM12) | (1 << WGM13);  
  
  // No prescaling (prescaler = 1)  
  TCCR1B |= (1 << CS10);  
  
  // TOP value for 20kHz PWM frequency  
  ICR1 = 799; // f_PWM = 16MHz / (1 * (1 + 799)) = 20kHz  
  
  // Set duty cycles  
  OCR1A = (ICR1 * 23) / 33; // BOOST duty on D9  
  OCR1B = (ICR1 * 5) / 15;   // BUCK duty on D10  
  
}  
void loop() {  
}
```



For 69.7% duty cycle, i.e for boost operation.

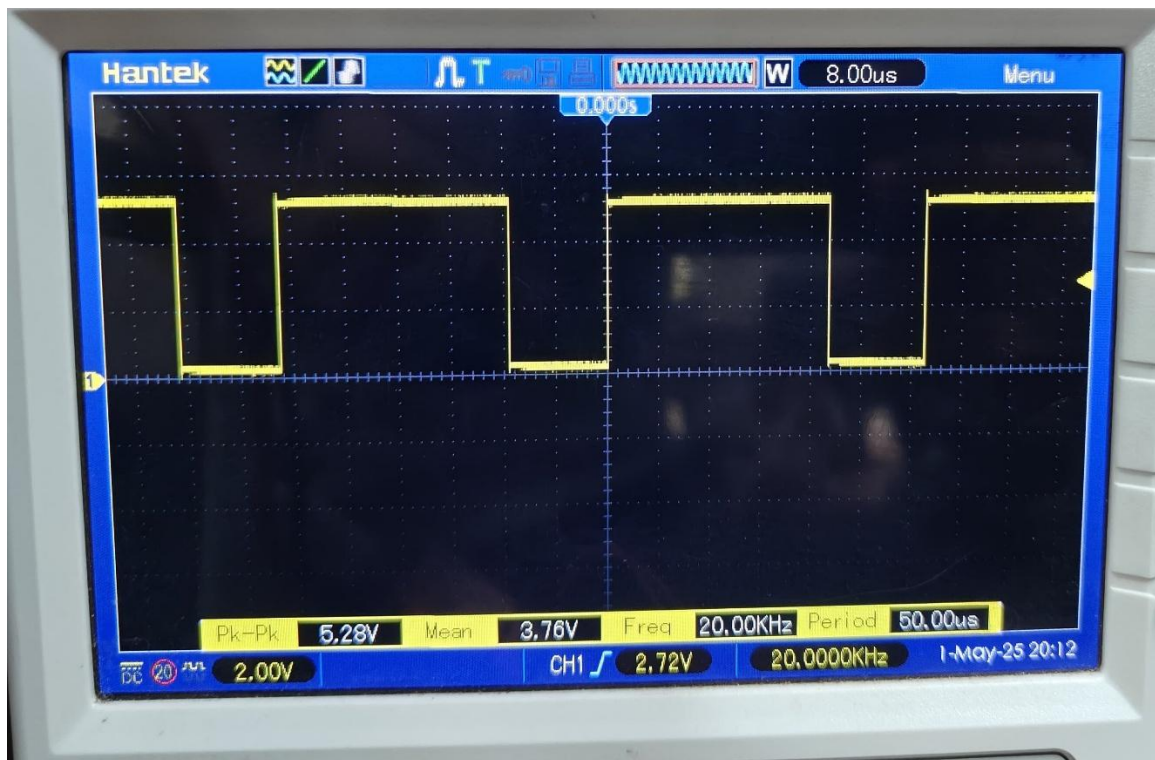

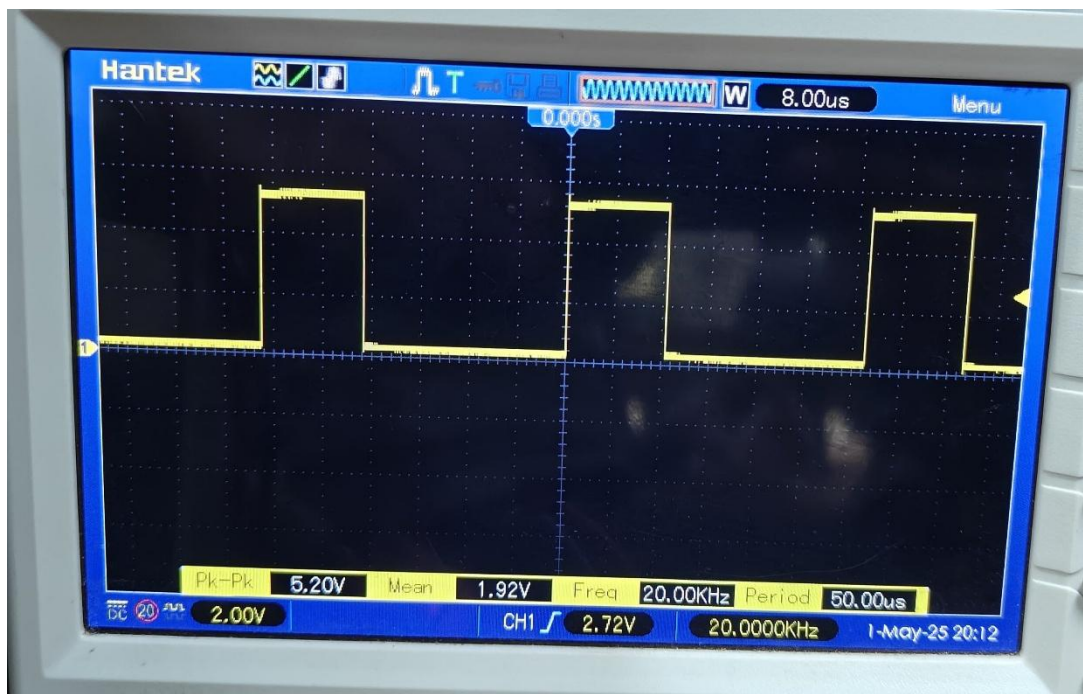
For 33.3% duty cycle, i.e for buck operation




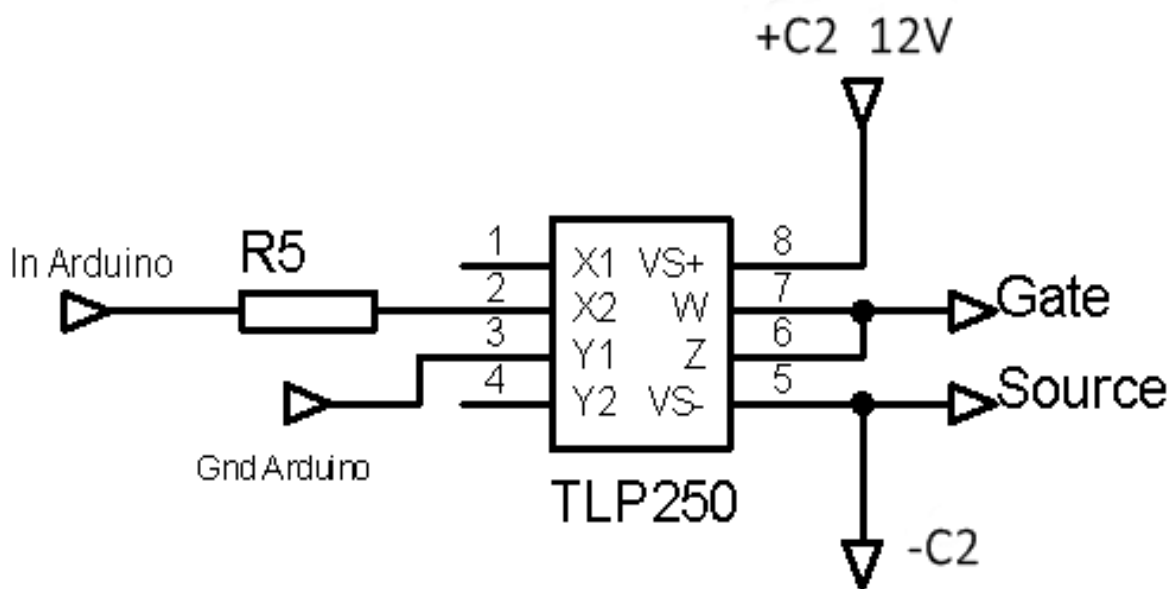
## Gate driver design

To drive the IRF740 as a high-side MOSFET, a 15 V gate signal was required—beyond the 5 V logic level provided by the Arduino. The **TLP250**, an opto-isolated gate driver, was chosen to safely translate 5 V logic to 15 V while providing necessary isolation between the control and power circuits, making it ideal for this high-voltage application.



### **Gate Resistor (Rg)**

Usually **1 resistor per gate** – used between the TLP250 output and the MOSFET gate.

$$R_g = V_{\text{drive}} / I_{\text{gate}}$$

It is chose to be 100  $\Omega$  for reduced EMI losses and proper switching speed

### **Pull-Down Resistor (Rpd)**

Connected between the **Gate and Source** of the MOSFET.


Typically 10k $\Omega$  is used

### **Bootstrap Capacitor (Cb)**


If you're driving a **high-side MOSFET** (like in a half-bridge), the **bootstrap capacitor** is used to provide gate voltage above the source.

But for TLP250, which is not bootstrap-based, the capacitor is usually a bypass capacitor between Vcc and GND

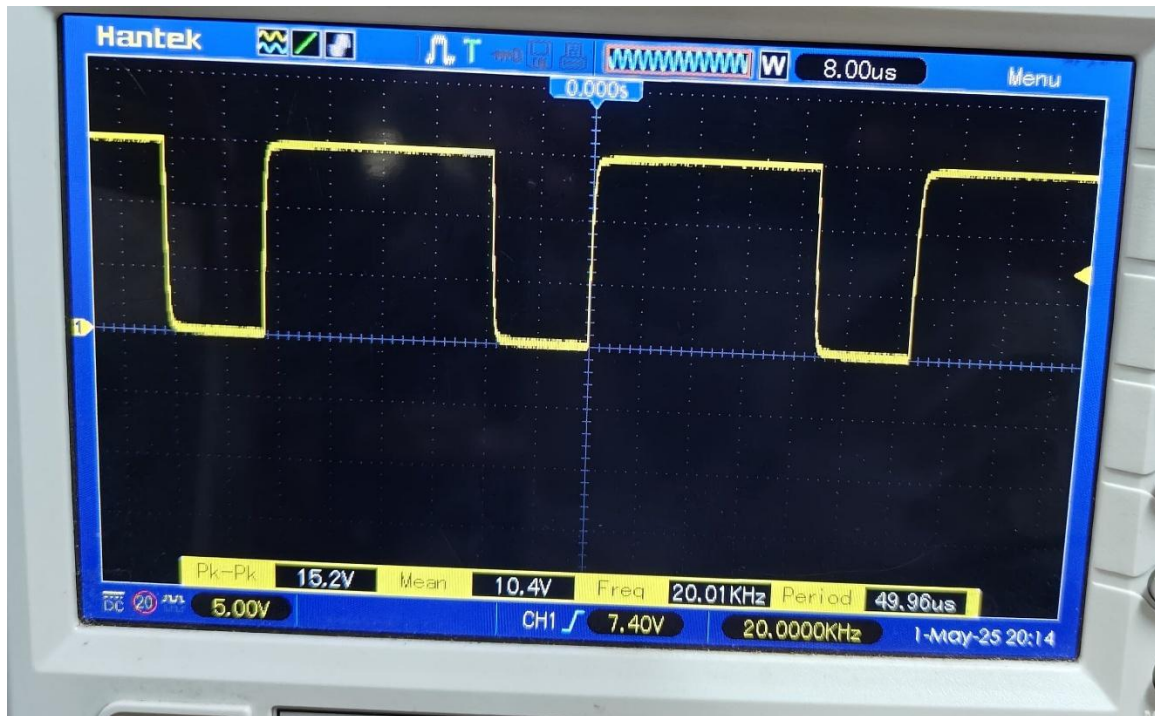Output from the gate driver for 69.7% duty cycle



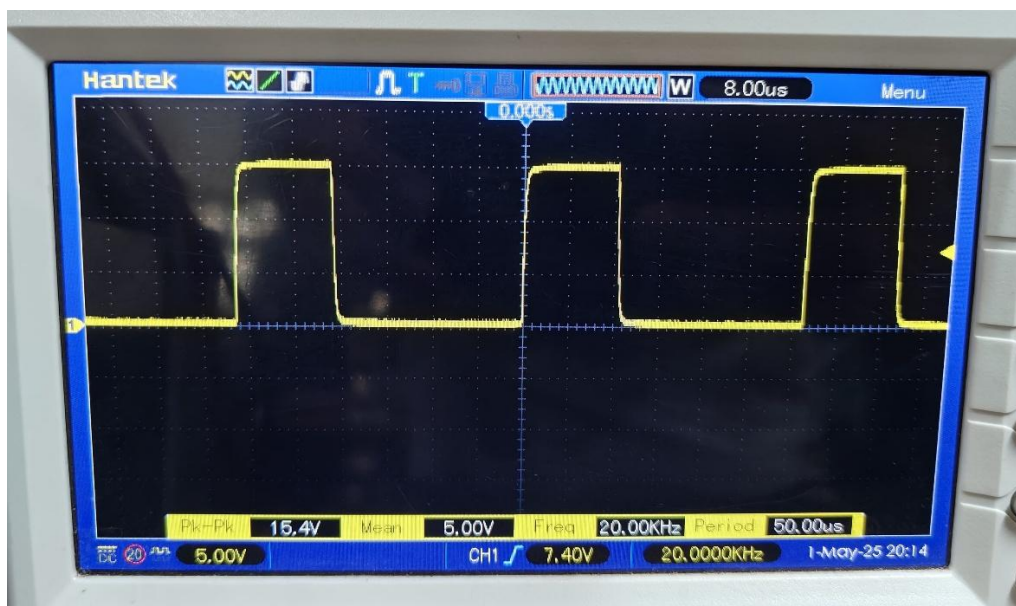Output from the gate driver for 33.3% duty cycle



## Inductor Design and Fabrication :

### **Objective:**

Design and fabricate a 4 mH inductor suitable for use in a buck-boost converter operating around 100V input, with capability for both step-up and step-down modes.

$$L = (\mu_0 \cdot \mu_r \cdot A \cdot N^2) / l$$

### **1. Core Selection:**

**Core Type:** EE55 ferrite core (MnZn material) chosen for high-frequency performance and minimal core losses.

#### **Core Parameters:**

- **A(Effective Area):**  $\sim 1.5 \text{ cm}^2$
- **L(Magnetic Path Length):**  $\sim 8.5 \text{ cm}$
- **B:**  $\sim 0.35 \text{ T}$
- **$\mu_r$ :**  $\sim 2000$  (assumed for gapped ferrite)

### **2. Inductance Calculation:**

- **Target Inductance (L):** 4 mH
- **Frequency:**  $\sim 20 \text{ kHz}$
- **Estimated Turns (N):**  $\sim 85\text{--}100$  turns (adjusted empirically based on actual inductance measured using LCR meter)
- **Wire:** AWG 20 enameled copper wire (current rating  $\sim 1.5\text{--}2 \text{ A}$  continuous)

### **3. Saturation Current Check:**


With the gapped core, a saturation current of around **1.5–2 A** was achieved, which was within expected limits for the converter's operation.

### **4. Fabrication:**

- **Winding:** 90 turns of AWG20 wire.



## Result:

### **Boost operation**

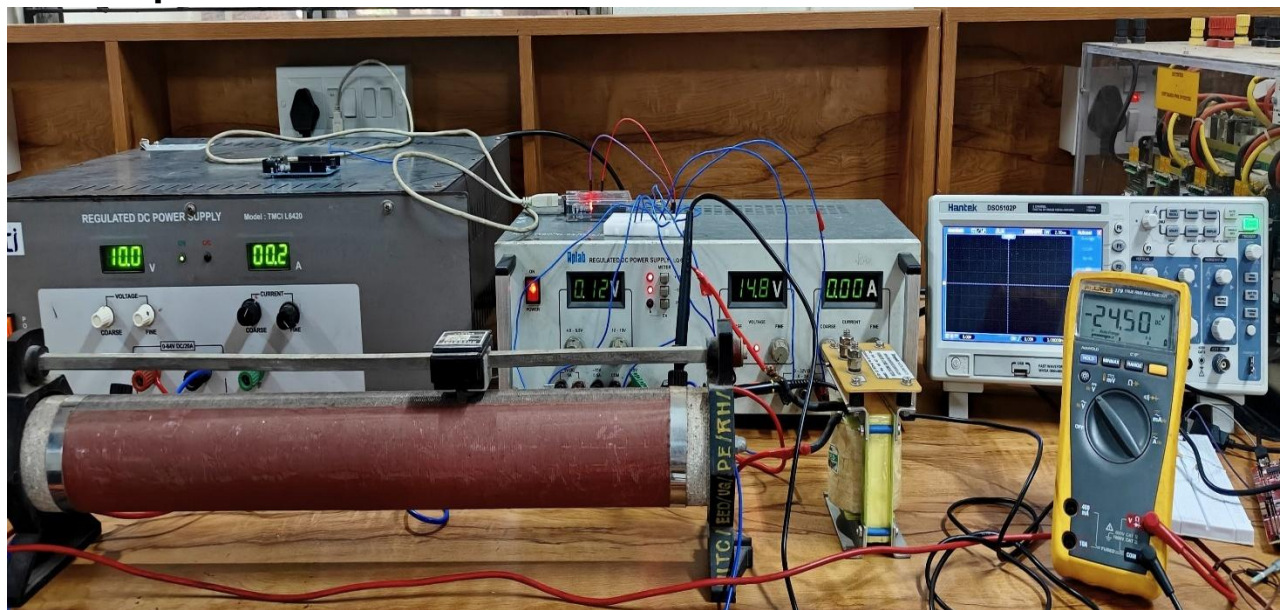



## Buck operation

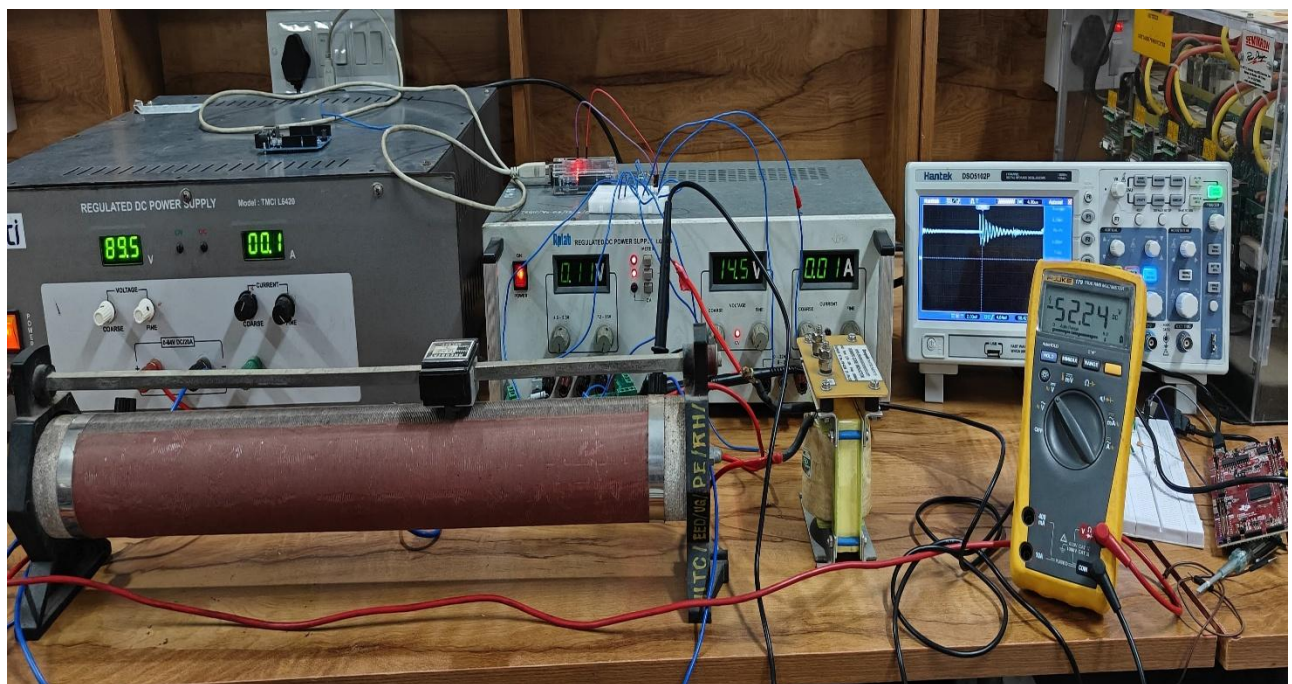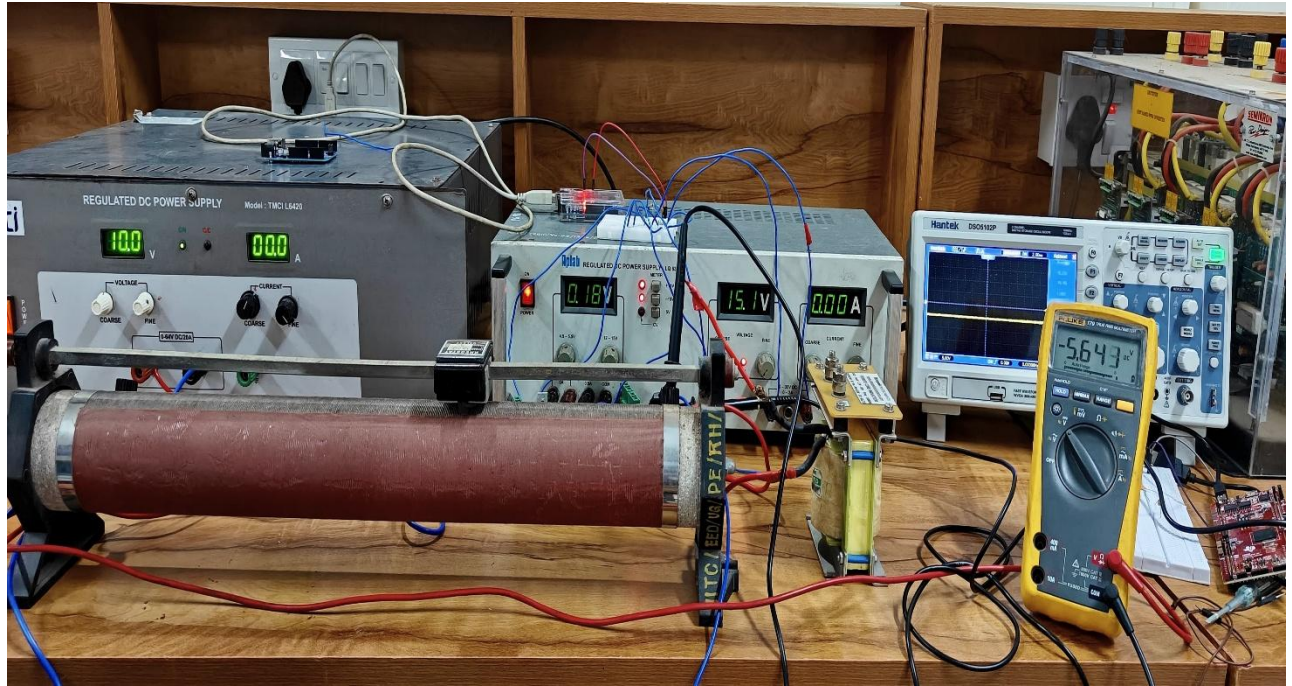

### Application:

A buck-boost converter is ideal in **UPS (Uninterruptible Power Supply) systems**. In **buck mode**, it steps down rectified AC ( $\sim 100$  V DC) to charge a **48 V battery bank**. In **boost mode**, during a power outage, it steps up the battery voltage ( $\sim 100$  V) to **230 V DC**, which is then inverted to AC to power connected devices. This dual functionality ensures reliable charging and uninterrupted power delivery in a single compact design.

**Conclusion:**

This project successfully demonstrates a buck-boost converter capable of regulating output voltage under varying input conditions using an IRF740 MOSFET driven by the isolated TLP250 gate driver. The converter design, including calculated inductor and capacitor values, ensures efficient energy conversion with acceptable ripple levels. Its practical relevance is evident in renewable energy systems and other applications requiring stable voltage from variable power sources.

-----THE END-----